


**Abdalrahman Ali Eltaher**  
**Group 2**  
**Assignment 1**

# •Q [1]


## ➤ The Code :

```
Q1.v
E:\> Deploma karem > Assignment_1 > Q1.v
1  /*this program is detected if A greater than '0010'
2   and less than '1000' the out is High else is Low*/
3
4  module detect_high(A,out);
5  input  [3:0] A;
6  output  out;
7  assign out = (A >4'b0010 && A<4'b1000)? 1:0;
8  endmodule
```

## ➤ The Wave :

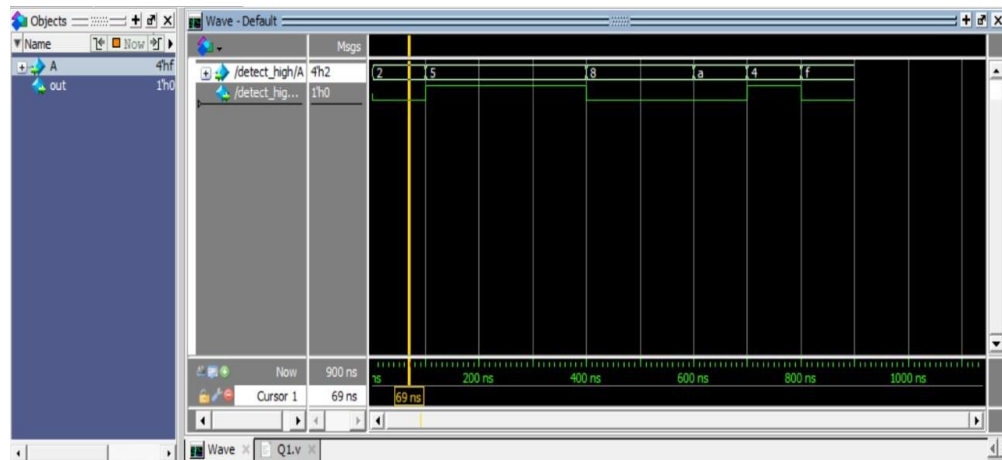

## ➤ The Schematic :


 


## •Q[2]


### ➤ Code :

```
1  /*this program creates XOR gate When two inputs have a same value
2  the output is Low and when they have A different value
3  the output is High. */
4
5  module XOR_gate(A,B,F);
6  input A,B;
7  output F;
8  assign F = A ^ B;
9
10 endmodule
```

### ➤ Wave:

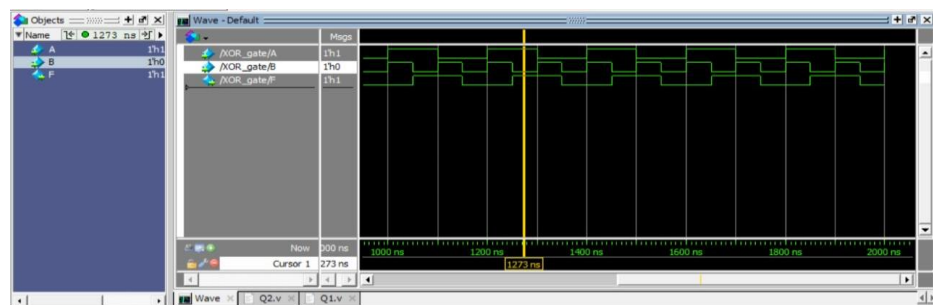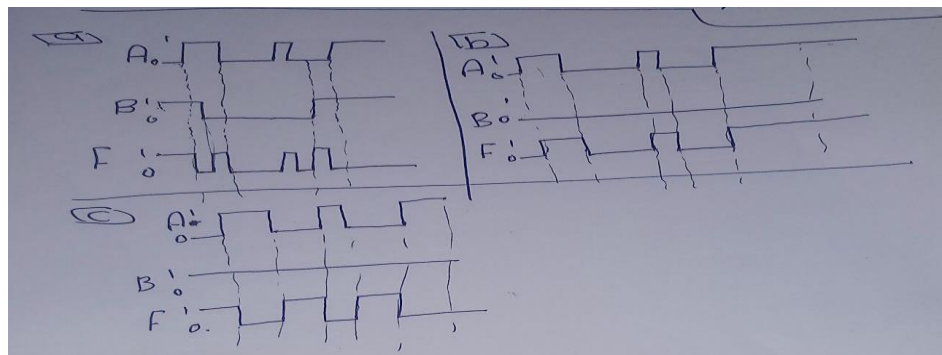

### ➤ Schematic :

 

## • Q[3]

➤ Code :

```

1  /*This program is a set of logic gates
2  to implement a specific function
3  and the output is equal to 1 when A=0 B=1, C=1*/
4  //-----
5  module logic_gate(A,B,C,F);
6  input A,B,C;
7  output F;
8  assign F = ((A ^ B) & (B ~^ C) & (C) );
9  endmodule

```

➤ Wave :




➤ Truth Table :

Truth Table

A	B	C	$A \oplus B$	$A \oplus B$	$[(A \oplus B) \cdot (A \oplus B) \cdot C]$
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	0

➤ Schematic :

 


## • Q [4]

- Yes, NOR gate can be replaced by the comparator .


### ➤ Code:

```
1 // NOR gate .
2 module nor_gate(A,F);
3 parameter N = 3 ;
4 input [N-1:0] A;
5 output F ;
6 assign F = ~| A ;|
7
8 endmodule
```

### ➤ Wave:

 

### ➤ Schematic:

 

# • Q[5]

## ➤ Code:


```

1  module ALU(A,B,A_invert,B_invert,Carry_In,operation,Carry_Out,Result);
2  input A,B,A_invert,B_invert,Carry_In;
3  input [1:0]operation;
4  output Carry_Out,Result ;
5  wire z1,z2,y0,y1,y2;
6  assign z1 = (A_invert == 1)? ~A:A;
7  assign z2 = (B_invert == 1)? ~B:B;
8  assign y0 = z1 & z2;
9  assign y1 = z1 | z2 ;
10 assign {Carry_Out,y2} = Carry_In+z1+z2;
11 assign Result = (operation == 0)? y0 :(operation == 1)? y1 :y2 ;
12
13 endmodule

```
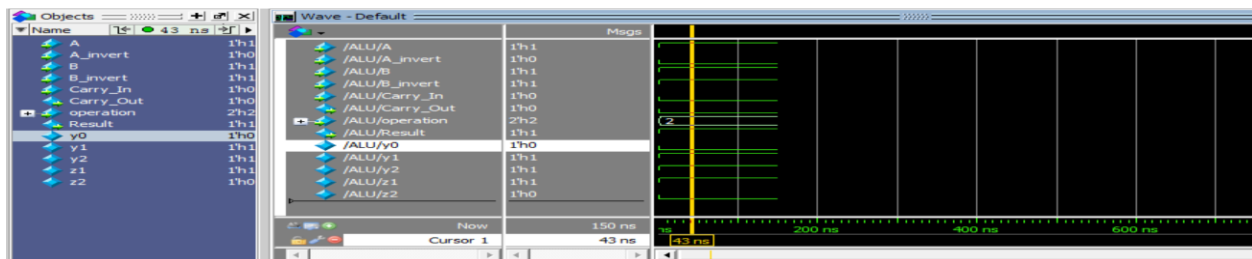
## ➤ Wave:

∴ A = 1, Ainvert=0 ∴ Z1=1 and ∴ B=1, Binvert=1 ∴ z2=0 .  
 ∴ y0=0, y1 = 1 and ∴ Carryin = 0 ∴ y2=1 and Carryout=0.  
 ∴ operation = 2'h2 ∴ Result = y2=1.



## ➤ Schematic :

